

Fig. 2. Variable modulation control, incorporated in the E200, allows increased r-f audibility without r-f overload and provides a means for checking demodulation capabilities of the second detector.

It is surprising to note that, although the average Service Man may be well equipped with modern test apparatus and is well versed in the operation of his instruments, not as much attention has been given, as should be, to the systematic application of these same units to other than their most obvious intents. This seems to be particularly true of the signal generator.

This one instrument is capable of forming the foundation of a complete servicing technique or system which will allow the localization of almost any receiver trouble. A signal generator of proper design can perform amazingly more useful functions than as a mere variable frequency source for alignment.

No claim is made that the system de-

# SIGNAL SUBSTITUTION

By G. N. GOLDBERGER

PRECISION APPARATUS COMPANY

system is, on the whole, an orderly accumulation of many methods which you or the next man may have at one time or other employed in the solution of puzzling radio problems.

What is to follow is only a small idea of the possibilities of this servicing method, and confined to but a few examples. The system is founded on fundamental factors and its application is limited only by the operator's own knowledge, ability and confidence in what he is doing.

For the sake of simplicity let us confine ourselves to a common superheterodyne receiver, such as that shown in Fig. 1. The same system of attack, however, is applicable to all receivers regardless of variations. This receiver, let us say, has been brought to us for service with no more of a lead as to the nature of the trouble other than "Fix it, it doesn't work."

## Tube Testing

It is a good policy to test all the tubes first. The immediate isolation of a shorted tube (or the finding of a very weak oscillator) is at times the entire solution to the problem. The fact, however, that all the tubes have passed this initial test does not always definitely

Many an oscillator tube can pass both emission and dynamic types of tests and still not function in a receiver, especially if the oscillator circuit accidentally or intentionally requires a tube with high hop. Gassy tubes, on the other hand, will initially test perfectly, but if allowed to operate in the receiver or tube tester, will start to draw grid current or otherwise go sour.

## Power Supply

If the tubes test ok in the tester, we can temporarily eliminate them as possible sources of trouble and proceed to the next part of the test.

The use of an ordinary multirange meter in conjunction with manufacturer's specifications will allow immediate determination as to whether the proper voltage is available at the power supply and at points A and B (Fig. 1). If the proper voltage is not obtainable, i.e. no reading, excessive reading or below normal, the type of reading obtained will indicate the nature of the trouble. Little difficulty is ever experienced in cases so simple as this. However, should the difficulty not be directly associated with the power supply, and should the operator not desire to make a systematic stage by stage voltage test, the trouble will definitely appear during the systematic signal analysis.

## Audio Stages

Let us now set our signal generator for the 400-cycle sine-wave output and start the analysis right at the output transformer. The instrument employed must have sufficient signal output of good wave form to allow direct application at the point C (Fig. 1). At this point both the audio output transformer and the speaker are simultaneously tested. By starting with a sine-wave signal a speaker deficiency such as a slight rubbing of the voice-coil frame to pole piece, with consequent distortion, is readily detected. At the same time the output transformer is tested directly. In all these tests (and in those which follow) the return probe is connected to the receiver chassis.

Moving the audio probe to D requires a reduction in the signal generator a-f attenuator proportionate to the gain of the output tube. No signal (as evidenced by a silent speaker, monitored by the multimeter) localizes the difficulty, the exact nature of which can be readily detected by a multimeter test in this small portion of the receiver. It could

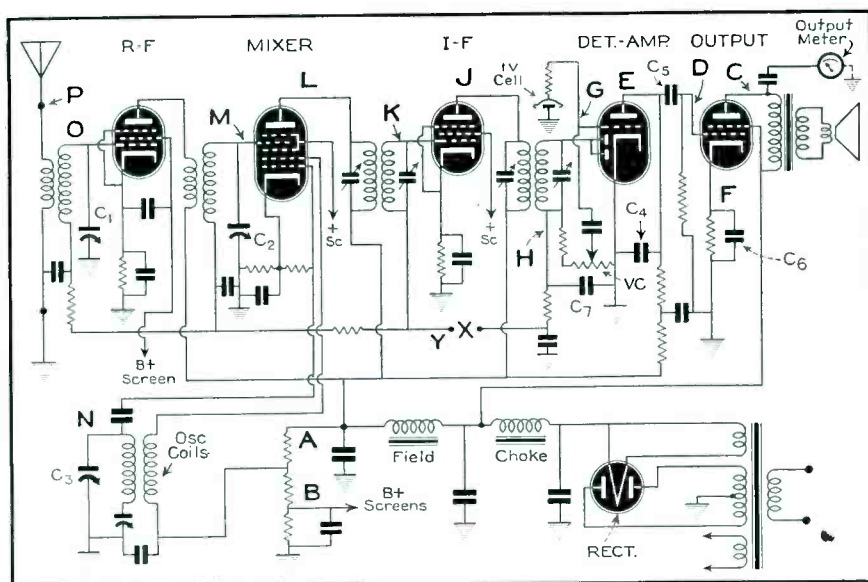


Fig. 1. Signal substitution provides a servicing technique for the systematic location of receiver faults.

scribed in this article is radically new or revolutionary. It is simply well grounded technique and application based on a few everyday principles. No additional equipment is required than what would normally be on hand in the average service shop . . . a signal generator, multimeter and a tube tester. The

eliminate them as a possible source of trouble. No tube tester available to the Service Man is infallible and actual try-out in the receiver is the final determining factor.







# SERVICING by S

With "PRECISION" BAS

## "S-S-S" == "SERVICING BY SIGNAL SUBSTITUTION"\*

● It is the modern, ECONOMICAL key for the solution of your daily service problems . . . there is nothing complex to learn, no need to wish for a third arm and hand, no extraneous equipment to purchase . . . a new systematic method of true DYNAMIC SIGNAL ANALYSIS based entirely on simple fundamentals . . . employing ONLY BASIC TEST EQUIPMENT as is normally absolutely required in the service laboratory: a reliable dynamic mutual conductance type tube tester such as PRECISION Series 910, an accurate wide-range sensitive multi-tester such as PRECISION Series 852, and the PRECISION Series E-200 laboratory Signal Generator, SPECIFICALLY DESIGNED for the purposes of "SERVICING BY SIGNAL SUBSTITUTION."

"S-S-S" with PRECISION Basic Test Equipment, provides a new high in simple rapid localization and determination of receiver troubles . . .

"S-S-S" is UNIVERSAL . . . the same simplified approach applies equally as well to all receiver types regardless of age, make, design, number of tubes, etc. . . .

"S-S-S" gives you unsurpassed dollar value and service from BASIC TEST EQUIPMENT ONLY!

"S-S-S" in a single systematic dynamic attack, completely covers the entire problem, with the receiver in ACTUAL OPERATION . . .

"S-S-S" provides complete stage-by-stage check-up, trouble shooting and alignment directly from the speaker to antenna post, in one consecutive series.

To mention only a few of the innumerable features of "S-S-S" . . . ● DIRECT R.F. AND I.F. gain-per-stage measurements . . . ● Finds uncoupled, dead or mistracking oscillators . . . ● Quickly locates shorted or open I.F. and R.F. transformer turns . . . ● Picks out open R.F. or audio by-pass and coupling condensers . . . ● Immediately tells necessary direction of I.F., R.F., and oscillator trimmer or padder alignment, etc.

### FREE

Now in preparation and FREE (as soon as off the press) to all PRESENT OWNERS and FUTURE PURCHASERS of Series E-200, a new illustrated text describing this amazingly economical and simplified speed approach to receiver adjustment problems, "Serving by Signal Substitution."

\* "Servicing by Signal Substitution" Copyright 1940 by Precision Apparatus Co., Brooklyn, New York.



## PRECISION T

Standard of Accuracy


SE

PRECISION APPARATUS COMPANY • 647 Kent Avenue, Brooklyn, N.Y.



# SIGNAL SUBSTITUTION\*

## BASIC TEST EQUIPMENT

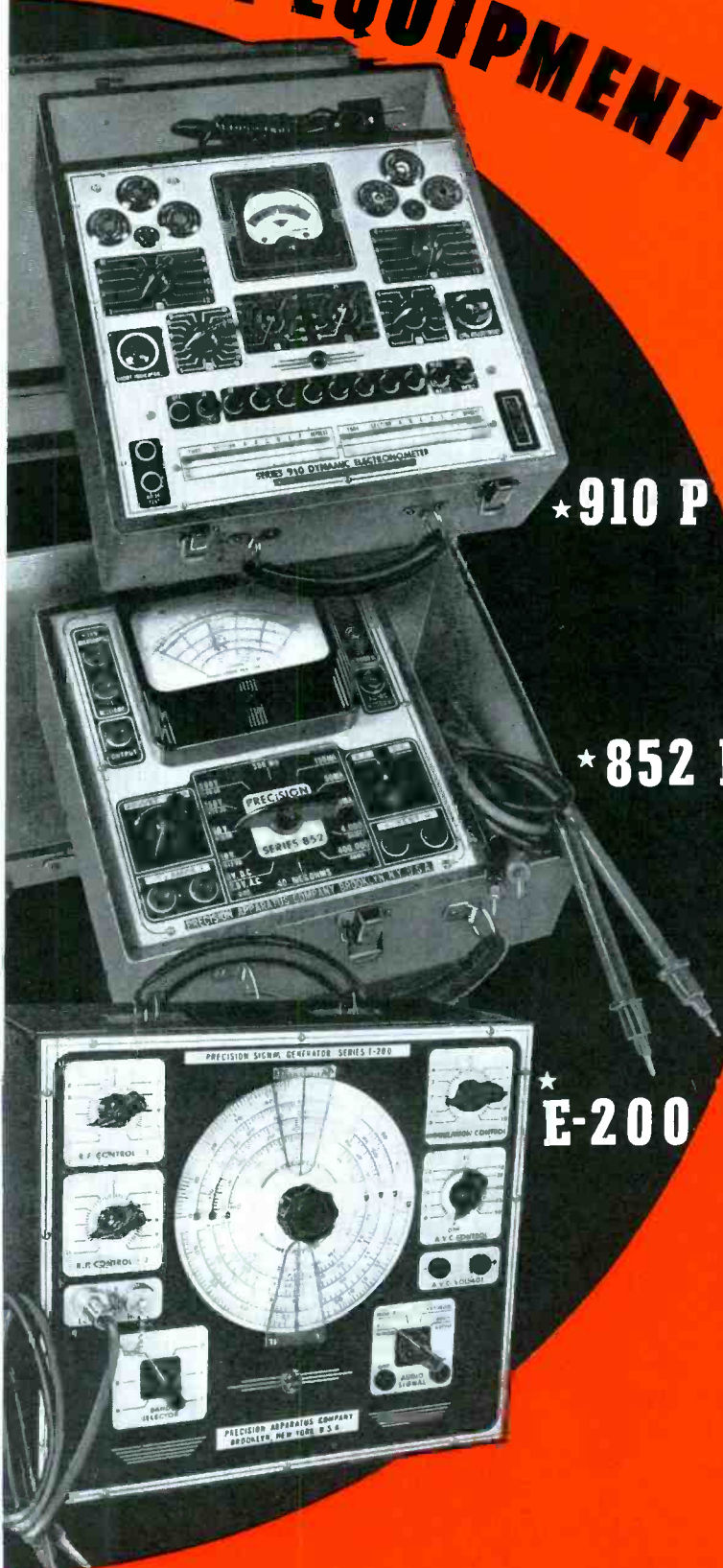

★ 910 P

★ 852 P

★ E-200

### ★ Series 910

#### DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

The first step in "S-S-S" is the rapid, unfailing selection and elimination of defective tubes. The PRECISION series of Dynamic Mutual Conductance Type Tube Testers. (Series 910, 912, 915, 920 or 922) will permanently and efficiently remove the "Question Mark" from your tube test problems.

##### QUICK FACTS:

- A DYNAMIC MUTUAL CONDUCTANCE TYPE TUBE TESTER, which in one operation, effectively tests all radio receiving tubes for both MUTUAL CONDUCTANCE and CATHODE STRUCTURE • TESTS ALL LATEST TUBE TYPES and ALL FILAMENT VOLTAGES • AUTOMATIC PUSH BUTTON SYSTEM for non-obsoluscent free-point tube analysis • DUAL FREE-POINT FILAMENT TERMINAL SELECTION • VISIBLE FILAMENT CONTINUITY TESTS • SPECIFIC INDIVIDUAL LOAD AND VOLTAGES: APPLIED TO EACH ELEMENT OF TUBE UNDER TEST • VARYING A.C. SIGNAL applied to control grids • METER READS IN PLATE CIRCUIT • OPEN ELEMENTS: Instantly shows up any tube having an open element • INDIVIDUAL TESTS for each section of multi-section tubes • HOT CATHODE LEAKAGE TESTS • HOT INTER-ELEMENT SHORT TESTS • NOISE TESTS • BALLAST TESTS • PILOT LIGHT TESTS • BUILT-IN DOUBLE WINDOW ROLLER TUBE CHART. New charts furnished at no charge • MICRO-LINE ADJUSTMENT, no arbitrarily tapped transformer • PILOT LIGHT (ON-OFF) INDICATOR: FUSED LINE PLUG • TELEPHONE CABLED WIRING EMPLOYED THROUGHOUT • ACCURACY closely maintained by use of factory adjusted and sealed individual calibrating controls • GUARANTEED for ONE FULL YEAR.

PRECISION Series 910P, (illustrated), housed in attractive, removable hinged cover, hardwood, walnut finished carrying case, with built-in tool compartment; also available in counter or standard panel mount. Dealer net price, \$33.95

Series 910MCP, housed in fine dull black wrinkle finished, open face metal cabinet, same as illustrated for Series E-200; dealer net price \$29.95

### ★ Series 852

#### SUPER-SENSITIVE TESTER

39 Range A.C.-D.C. volt-ohm-decibel-milliammeter-ammeter . . . Including ranges to 5000 volts A.C.-D.C., 50 microamperes, 10 AMPERES AND 40 MEGOHMS.

The high sensitivity of 20,000 ohms per volt D.C. affords reliable measurements in modern radio and television circuits wherein only minute current drain of the measuring instrument can be tolerated.

A single Master Rotary Range Selector permits simplified rapid check of voltage, current, resistance, etc., in troublesome stages, quickly localized through "S-S-S".

##### QUICK FACTS:

- SEVEN D.C. voltages ranges at 20,000 ohms per volt to 5000 volts • SEVEN A.C. voltage ranges at 1000 ohms per volt to 5000 volts • EIGHT E.C. current ranges: 0-50 microamps to 0-10 AMPS • THREE RESISTANCE RANGES to 40 MEGOHMS powered by self-contained batteries • SEVEN DECIBEL RANGES FROM -12 to + 69DB • SEVEN OUTPUT RANGES to 5000 volts • METER: Large, modern 4 1/2" "PRECISION" square meter with cobalt magnet; accurately machined soft-iron pole pieces; double jeweled D'Arsonval 50 microampere movement • WIRE-WOUND SHUNTS AND METALLIZED MULTIPLIERS BOTH OF 1% ACCURACY.

PRECISION Series 852P (illustrated) housed in attractive, removable hinged cover, hardwood walnut finished carrying case with built-in tool compartment; dealer net price (complete with batteries and test leads) \$41.95

Standard panel mounted Series 852PM (complete with batteries and test leads), \$42.95  
Series 852L, housed in hardwood open, face, walnut finished carrying case; dealer net price (complete) \$39.95

### ★ Series E-200

#### LABORATORY SIGNAL GENERATOR

The key to "S-S-S" . . . the simplified method of dynamic receiver analysis, employing ONLY BASIC TEST EQUIPMENT.

Not only an unsurpassed, efficient, laboratory Signal Generator for purposes of alignment but also SPECIFICALLY DESIGNED as the heart of "Servicing by Signal Substitution" and priced easily within the reach of every progressive radio service engineer.

##### QUICK FACTS:

- SIX BANDS: Full coverage from 110 K.C. to 72 M.C. Direct reading. • ACCURACY: Uses the new 6SJ7 in the "PRECISION" developed "UNIT OSCILLATOR"—buffer amplifier construction, insuring MAXIMUM 1% DEVIATION ON ALL BANDS • LARGE FULL VISION 6 INCH DIAL with ball-bearing drive system • 1000 POINT VERNIER SCALE plus Twin Engraved Hair-Line Indicators afford readings free from parallax • POSITIVE DUAL R.F. NON-REACTING ATTENUATORS . . . CALIBRATED for direct gain measurements in "S-S-S" • COAXIAL OUTPUT CABLE . . . provides low-loss connections for all "S-S-S" requirements • 4 SIGNALS: Unmodulated R.F.; Modulated R.F.; Externally Modulated R.F. (Freq. or Amp.); 400 Cycle Audio Output • 400 CYCLE SINE-WAVE OSCILLATOR MODULATOR . . . Independently Controlled, providing zero to over 60 volts audio signal for all "S-S-S" purposes • VARIABLE MODULATION CONTROL . . . provides 0-100% modulation AT WILL • THE A.V.C. SUBSTITUTION NETWORK . . . overcomes serious alignment troubles by supplying its OWN DIRECTLY CALIBRATED A.V.C. VOLTAGE • HAND CALIBRATION: Each instrument INDIVIDUALLY calibrated against precise laboratory standards • FULLY LICENSED UNDER PATENTS OF AMERICAN TELEPHONE AND TELEGRAPH COMPANY.

PRECISION Series E-200 (illustrated) housed in attractive fine dull black wrinkle finished, open face heavy gauge metal cabinet. Dealer net price (complete with tubes and coaxial output cable) \$35.95

Also available in standard panel mount—complete \$31.95

More than 40 models in the PRECISION 194G LINE . . . 15 Mutual Conductance Tube Tester and Set Tester models ranging in price from as low as \$29.95 . . . 16 Multi-Range Tester models from as low as \$10.95 . . . Signal Generators from \$24.95 . . . etc. . . See them at your local distributor . . . Ask for the PRECISION TEST EQUIPMENT 194G CATALOG.

## TEST EQUIPMENT

THEM AT YOUR JOBBER

Export Division: 458 Broadway, N.Y.C., U.S.A., Cables: MORHANEX



## ONE TEST INSTRUMENT You know is a VALUE!

**RCP Model 308**

(Series D)

**ONLY \$25.95**

**DEALER NET**

It's called the Sales Promoter, so you know it means business. And it's built by RCP, so you know it's a value! But never in RCP Test Equipment history has appearance counted for more... never has engineering reached a stage so advanced... never has value-giving been greater. You have only to check the features and low price of Model 308 (Series D), compare it with other equipment, to discover how much more for your money RCP offers.



### JUST LOOK AT ALL THESE MONEY-MAKING FEATURES!

- ★ Extra-large 9-inch Jumbo meter
- ★ Famous Dynoptimum Test Circuit
- ★ Tests the new miniature tubes
- ★ Spare sockets for new developments
- ★ Checks pilot lights, headlights, miniature lights
- ★ Rapid, simple tests for quality, shorts, etc.
- ★ Individual tests of all sections of rectifiers and multi-purpose tubes
- ★ Noise and hum tests for tubes showing "good"

SERVICEMEN EVERYWHERE are making more money with RCP Test Equipment. And saving money, on the initial cost! By all means, buy quality, but be smart and get value. Ask for RCP Test Instruments. If your jobber cannot supply you, send at once for new FREE Catalog No. 122.

**RADIO CITY**  
PRODUCTS CO. INC.  
88 PARK PLACE, N. Y. C.

### SIGNAL SUBSTITUTION

(Continued from page 15)

the avc threshold, it will not be functioning with optimum performance under normal conditions.

If we were to substitute a fixed bias in place of the varying avc voltage, and were able to adjust this fixed bias to any desired value equal to that which normal local signals develop in the diode, we could then align and test this receiver under practically true operating conditions, and without detrimental avc interference.

The signal generator employed in

developing this article furnishes a variable bias voltage between zero and fifty volts specifically for avc substitution. All that is required is to open the avc circuit at X, and connect the substitute bias with the negative end toward Y. Alignment of the receiver can then be carried out as if no avc were present.

With the probe at K, the i-f stage can be analyzed, the output section of the i-f transformer adjusted and the diode winding alignment rechecked. By-pass condenser efficiency can be determined in the manner suggested for the audio stages, and shorted turns can be detected readily as mentioned above.

At the same time i-f and r-f gain per stage measurements may be made if the generator employed is provided with a calibrated output control.<sup>1</sup> This is done briefly as follows: With the r-f probe at J, set the r-f attenuators and modulation control to give some arbitrary reading on the output meter near the middle of the scale. Note the attenuator setting. Shift the probe to K. Reduce the attenuator setting until the output meter indicates the same reading as that obtained when the probe was at J. Again note the attenuator setting. The ratio of the two settings indicates the gain of the stage directly.

The probe at L tests the transfer of signal through coil to K, just as the probe at J checks the signal through to the diodes. Placing the probe at M, and still employing the 456-kc signal, allows complete alignment of the input i-f transformer and also allows check of operation of the first detector at the intermediate frequency.

### R-F and Oscillator Stages

We are now ready for a complete test and adjustment of the first detector and oscillator. Set the receiver dial to the high end of the broadcast band, about 1500 kc, and apply the r-f probe to M with the generator set for 1500 kc, 400-cycle audio modulated, output. If the oscillator is oscillating and tracking, the audio tone should be heard from the set's speaker. If no signal is heard the oscillator should be checked first. It should be oscillating at 456 kc plus the dial reading (456 plus 1500) or 1956 kc. If the oscillator is oscillating but not tracking, the signal should be heard from the speaker when the generator dial is rocked around the 1500-kc position. If the oscillator is not oscillating at all, regardless of what generator setting is used, no signal will be heard in the speaker.

To check this, connect the generator probe at N and an antenna at M, switch off the generator's audio modulation

and tune it to approximately 1956 kc. Attempt to tune in a station in this manner using the signal generator as a substitute for the set's oscillator stage.

In some cases, where a receiver employs a separate oscillator tube coupled to the first detector through a small condenser, the condition of this condenser can be determined by placing the probe before and after the condenser. If the condenser is open or a lead broken the signal will appear only when the probe is at the mixer side of the condenser.

Once having ascertained that the first detector and oscillator are working, the probe may then be advanced to O where the 1500-kc signal is again applied and the first-detector trimmer adjusted. The r-f stage gain may be measured, if desired, in the same manner as outlined for the i-f stage. If no further difficulties exhibit themselves during this test, the probe is finally placed at P, and if the antenna coil, leads, etc., are continuous and no turns shorted, we proceed with the low-frequency padder adjustments and our set is complete.

It is realized that, as presented, things may appear rather sketchy, however, space limitations do not permit extended treatment. Nevertheless, it is hoped the reader has been able to formulate in his own mind the extensive application to which basic test equipment may serve, and how one's problems can thereby be systematically approached and solved.

### HOME RECORDING

(Continued from page 13)

a bias cell. The mike gain control is in the plate of the preamplifier. Note the mixer circuit; one side is fed from the mike gain control and the other from deck No. 1 bringing in radio programs from the diode detector or phonograph. A conventional tone control is used.

The Lafayette S53, a 9-tube push-pull combination radio recorder (see Fig. 5) switches to any one of 5 functions by means of a 5-position, 4-deck rotary switch. A 6SQ7 preamplifier is used for microphone recording and p-a applications. The 6U5 visual indicator tube is used both as a resonance indicator and as a level indicator during recording.

In p-a applications it is possible to reduce, or even eliminate acoustic feedback by providing avc in the audio amplifier. Too much avc will spoil the quality and cause excessive volume compression, but a certain amount will help obtain a proper input level.

Automatic record changer phonographs are coming out with recorder

<sup>1</sup>"Gain Measurements in R-F and I-F Stages," by Jack Avins, SERVICE, May, 1937, p. 273.